

Sequential Circuits in Verilog

Verilog Module Structure

Module STARTING

```
module design
(
  input [2:0] data,
  output [2:0] result
);
```

Module name portlist, port declaration
parameter declarations

```
reg reset_n, clk;
reg done;
reg FF_Q, FF_D;
integer i;
wire [2:0] data_in, data_out;
```

Declaration of wire and
reg variables

```
alg_module alg_instance (
  .clk (clk),
  .reset_n (reset_n),
  .d_in (data_in),
  .d_out (data_out)
);
```

Instantiation of
other module

```
assign data_in = 3'b001 + data;
assign result = data_out ^ data_in;
```

Continuous statements
or Data flow statement

```
initial begin
  forever #(5) clk=~clk;
end
```

Initial block:
blocking assignments

always block:
Non-blocking
assignments

```
always @(*) begin
  done=0;
  if ( start==1 ) begin
    done=1;
  end else if ( start==0 ) begin
    done=0;
  end else begin
    done=1;
  end
  case(FF_D)
    1'b0: begin
      FF_D=0;
    end
    1'b1: begin
      FF_D=1;
    end
  endcase
end
```

always block:
Non-blocking
assignments

```
always @ ( posedge clk or negedge reset_n) begin
  if (reset_n ==0) begin
    FF_Q <= 0 ;
  end else begin
    FF_Q <= FF_D;
  end
end
```

tasks and
functions


```
task decrypt_task ;
endtask
```

Module ENDING

endmodule


D Flip-Flop
 
```
module D_ff(input clk, input d, output reg q);  
    always @ (negedge clk)  
        q <= d; // pronounced "q gets d"  
endmodule
```



D Flip-Flop with Asynchronous Reset
 
```
module D_ff (input clk, input reset, input d, output reg q);  
    always @ (negedge clk, posedge reset)  
    begin  
        if (reset == 1) q <= 0; // when reset  
        else q <= d; // when clk  
    end  
endmodule
```



D Flip-Flop with Synchronous Reset

```
module D_ff (input clk, input reset, input d, output reg q);
```

```
always @ (posedge clk)
```

```
begin
```

```
    if (reset == 1) q <= 0; // when reset
```

```
    else q <= d; // when clk
```

```
end
```


```
endmodule
```

D Flip-Flop with Enable and Reset

```
module D_ff (input clk, input reset, input d, input en, output reg q);  
    always @ (negedge clk, posedge reset)  
    begin  
        if (reset == 1) q <= 0; // when reset  
        else if (en) q <= d; // when enable and clk  
    end  
endmodule
```

T Flip-Flop
 
```
module T_ff (input clk, input reset, output q);  
  wire d;  
  D_ff dff1 (clk, reset, d, q);  
  not n1(d,q);  
endmodule
```



Structural Model : 4-bit Counter

```
module ripple_carry_counter (q, clk, reset);
```

```
output [3:0] q;
```

```
input clk, reset;
```


```
    T_ff tff0(q[0], clk, reset);
```

```
    T_ff tff1(q[1], q[0], reset);
```

```
    T_ff tff2(q[2], q[1], reset);
```

```
    T_ff tff3(q[3], q[2], reset);
```

```
endmodule
```

 

Finite State Machine

- Each FSM consists of three separate parts:
 - next state logic
 - state register
 - output logic




FSM Verilog Implementation

```
module FSM (q, i, clk, rst);  
  input clk,i, rst;  
  output q;  
  reg q;  
  reg [1:0] state, nextstate;
```

//The parameter descriptions are optional, it makes reading easier
 
```
parameter S0 = 2'b00, S1 = 2'b01,S2 = 2'b10;
```



output

S0 -> 0


S1 -> 0

S2 -> 1

FSM Verilog Implementation: 3-Always Block


```
module fsm (q, i, clk, rst_n);
    input i, clk, rst_n;
    output q;
    reg q;
    reg [1:0] state, next_state;
    parameter s0=2'b00, s1=2'b01, s2=2'b10;

    always @(posedge clk or negedge rst_n)
        if(rst_n==0)
            state <= s0;
        else
            state <= next_state;
    always @(*) begin
        next_state=s0
        case(state)
            s0: begin
                q=0;
                if ( i==1'b1)
                    next_state= s1;
                else
                    next_state=s0;
            end
            s1: begin
                q=0;
                if ( i==1'b1)
                    next_state= s2;
                else
                    next_state=s0;
            end
            s2: begin
                q=1;
                if ( i==1'b1)
                    next_state= s2;
                else
                    next_state=s0;
            end
        end
    end
end
endmodule // fsm
```

 



This is the recommended implementation of FSM.

 Last always (output) can be coded with assign statement



FSM Verilog Implementation: Single Always Block

```
module fsm(q, i, clk, rst);  
  input i, clk, rst;  
  output q;  
  reg q;  
  reg [1:0] state;  
  parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;  
  
  always @(posedge clk or posedge rst)  
    if (rst) begin  
      state <= s0; q <= 1'b0;  
    end else begin  
      case (state)  
        s0: if (i == 1'b1) begin  
              state <= s1;  
              q <= 1'b0;  
            end else begin  
              state <= s0;  
              q <= 1'b0;  
            end  
        s1: ..  
        s2: ..  
      endcase  
    end  
end
```

  

output
S0 -> 0
S1 -> 0
S2 -> 1