 


Verilog

Verilog

- Verilog is a HARDWARE DESCRIPTION LANGUAGE (HDL)
- Offer a way to design circuits using text-based descriptions.
- HDLs are used to describe a digital system
- Not a programming language despite the syntax being similar to C
- Synthesized (analogous to compiled for C) to give the circuit logic diagram



Verilog Module Structure

Module STARTING

```
module design
(
  input [2:0] data,
  output [2:0] result
);
```

Module name portlist, port declaration
parameter declarations

```
reg reset_n, clk;
reg done;
reg FF_Q, FF_D;
integer i;
wire [2:0] data_in, data_out;
```

Declaration of wire and
reg variables

```
alg_module alg_instance (
  .clk (clk),
  .reset_n (reset_n),
  .d_in (data_in),
  .d_out (data_out)
);
```

Instantiation of
other module

```
assign data_in = 3'b001 + data;
assign result = data_out ^ data_in;
```

Continuous statements
or Data flow statement

```
initial begin
  forever #(5) clk=~clk;
end
```

Initial block:
blocking assignments

always block:
Non-blocking
assignments

```
always @(*) begin
  done=0;
  if ( start==1 ) begin
    done=1;
  end else if ( start==0 ) begin
    done=0;
  end else begin
    done=1;
  end
  case(FF_D)
    1'b0: begin
      FF_D=0;
    end
    1'b1: begin
      FF_D=1;
    end
  endcase
end
```

always block:
Non-blocking
assignments

```
always @ ( posedge clk or negedge reset_n) begin
  if (reset_n ==0) begin
    FF_Q <= 0 ;
  end else begin
    FF_Q <= FF_D;
  end
end
```

tasks and
functions



```
task decrypt_task ;
endtask
```

Module ENDING

endmodule

CODING IN VERILOG

  
- Breaking circuits into various building blocks called “module”
- Defining module
- Connecting various modules
- Communication between a module and its environment is achieved by using Ports
- Ports are of three types: input, output, inout



Verilog module


- A “Black Box” in Verilog with inputs, outputs and internal logic working.
- A Module in Verilog is declared within the pair of keywords **module** and **endmodule**. Following the keyword module are the module name and port interface list.
 
```
module my_module ( c, a, b );  
  input a, b;  
  output c;  
  ...  
Endmodule //comment
```




Instantiating module

 - `Module_name name(port1,port2,port3,.....);`



`or O1(w0,a,b);`

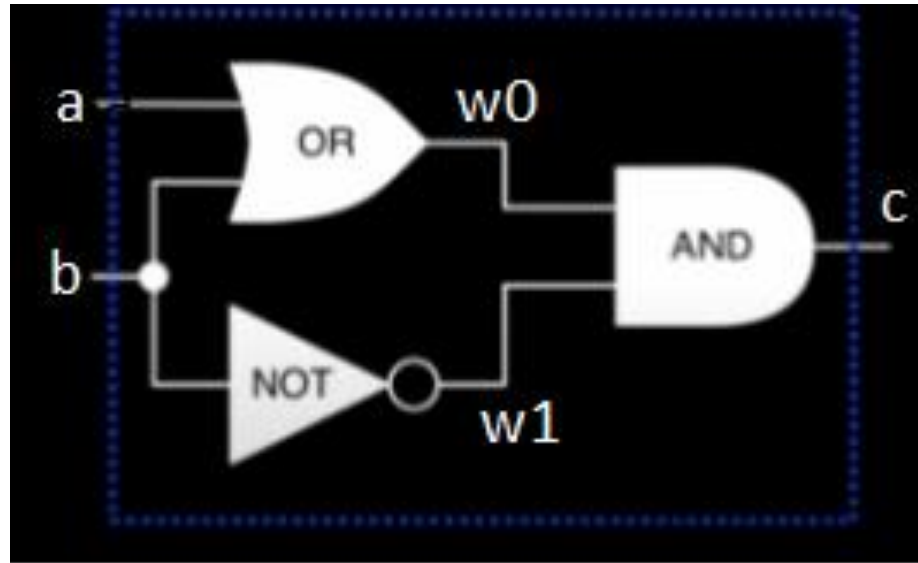


```
module cct (c,a,b);  
  output c;  
  input a,b;  
  or O1(w0,a,b);  
  not n1(w1,b);  
  and a1(c,w0,w1);  
endmodule //cct module
```


Order doesn't matter:
both describe the same circuit

```
module cct (c,a,b);  
  output c;  
  input a,b;  
  not n1(w1,b);  
  and a1(c,w0,w1);  
  or O1(w0,a,b);  
endmodule //cct module
```
 
```
module cct (c,a,b);  
  output c;  
  input a,b;  
  or O1(w0,a,b);  
  not n1(w1,b);  
  and a1(c,w0,w1);  
endmodule //cct module
```



Data Types

 

- wire


- Represents a physical connection, connects two points .
- Does not have a storage so it is used for designing combinational logic, (this kind of logic can not store a value).
- Default data type is wire (if you declare a variable without specifying reg or wire, it will be a 1-bit wide wire).

- Reg

- is a variable with a storage. If the register is assigned a value, it remains until it is assigned another value.
- it can be used for modeling both combinational and sequential logic.
- Reg data type can be driven from initial and always block.

Wire and Reg value levels

Each wire can be at 1 of 4 logic levels

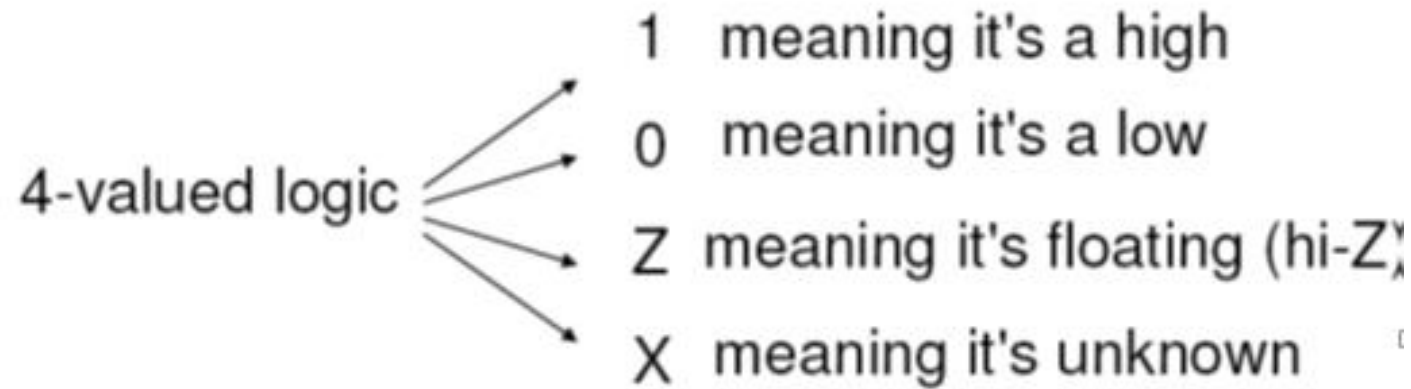

Constants

<size> '<base> <number>


number	b or B Binary	number in selected base
of <i>bits</i>	o or O Octal	may use _ as a spacer
	h or H Hex	0-extended with 0 or 1 msb
	d or D Decimal	x-extended with x msb
		z-extended with z msb

Constants

`<size>'<base> <number>`


<code>6'b010_111</code>	gives	<code>010111</code>
<code>8'b0110</code>	gives	<code>00000110</code>
<code>8'b1110</code>	gives	<code>00001110</code>
<code>4'bx01</code>	gives	<code>xx01</code>
<code>16'H3AB</code>	gives	<code>0000001110101011</code>
<code>24</code>	gives	<code>0...0011000</code>
<code>5'O36</code>	gives	<code>11 110</code>
<code>16'Hx</code>	gives	<code>xxxxxxxxxxxxxxxxxx</code>
<code>8'hz</code>	gives	<code>zzzzzzzz</code>

Bus notation

 


```
module adder4(c0, c1, c2, c3, a0, a1, a2, a3, b0, b1, b2, b3);  
  output      c0, c1, c2, c3;  
  input       a0, a1, a2, a3, b0, b1, b2, b3;
```

Bus notation

 

```
module adder4(c, a, b);  
    output [3:0] c;  
    input [3:0] a, b;
```

 
```
module adder4(c, a, b);  
    output [3:0] c;  
    input  [3:0] a, b;  
  
    xor lsb_xor(c[0], a[0], b[0]);  
endmodule
```



Direct assignment

```
assign x= b[3];  
assign mybus[3:0]=z[12:9];  
assign c[3]=a[1];
```


Modeling Types In Verilog

 

Model with submodules
and gates

=

Structural

Model with always
and initial blocks

=

*Behavioral
Procedural*


Model with
assign statements

=


*Behavioral
Dataflow*

 Example of structural (gate instantiation)

```
module smpl_circuit(A,B,C,x,y);  
  input A,B,C;  
  output x,y;  
  wire e;  
  and g1(e,A,B);  
  not g2(y,C);  
  or g3(x,e,y);  
endmodule
```



 
Example of continuous assignment (Dataflow modeling type)



```
module circuit_bln (x,y,A,B,C,D);  
  input A,B,C,D;  
  output x,y;  
    assign x = A | (B & C) | (~B & C);  
    assign y = (~B & C) | (B & ~C & ~D);  
endmodule
```

Example of Procedural modeling type

```
module circuit_bln (x,y,A,B,C,D);  
  input A,B,C,D;  
  output x,y;  
  reg x,y;  
  always@ (*)  
  begin  
    x = A | (B & C) | (~B & C);  
    y = (~B & C) | (B & ~C & ~D);  
  end  
endmodule
```

 

Logic simulation: generates waveforms

```
module smpl_circuit(A,B,C,x,y);  
  input A,B,C;  
  output x,y;  
  wire e;  
  and g1(e,A,B);  
  not g2(y,C);  
  or g3(x,e,y);  
endmodule
```

