

---


# **CPE 110408423**

## **VLSI Design**
 
### **Chapter 12: Array Subsystems**

Bassam Jamil

[Computer Engineering Department,  
Hashemite University]




# **Lecture 3: SRAM**

# Outline

---

- ❑ Memory Arrays
- ❑ SRAM Architecture
  - SRAM Cell
  - Decoders
  - Column Circuitry
  - Multiple Ports

# 12.1 Memory Arrays

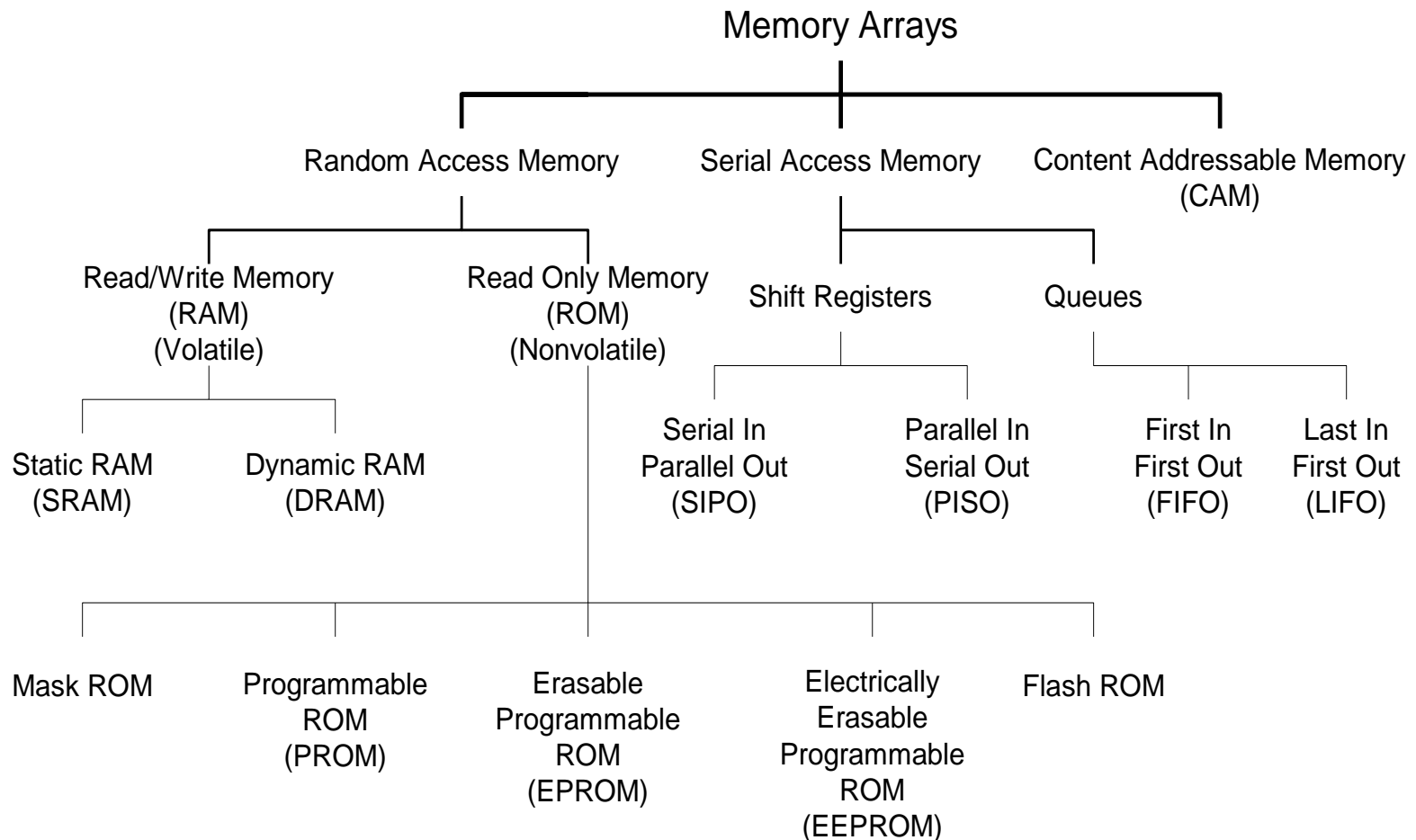

# Memory Arrays

- ❑ *Random access memory (RAM)* is accessed with an address and has a latency independent of the address.
- ❑ *Serial access memories (SAM)* are accessed sequentially so no address is necessary.
- ❑ *Content addressable memories (CAM)* determine which address(es) contain data that matches a specified key.
- ❑ Volatile vs. nonvolatile memory.
  - Volatile memory retains its data as long as power is applied,
  - nonvolatile memory will hold data indefinitely.
  - RAM is synonymous with volatile memory, while ROM is synonymous with nonvolatile memory.

# Volatile Memory

- ❑ The memory cells used in volatile memories can be divided into **static** structures and **dynamic** structures.
- ❑ **Static cells** use some form of feedback to maintain their state,
- ❑ **Dynamic cells** use charge stored on a floating capacitor through an access transistor.
  - Charge will leak away through the access transistor even while the transistor is OFF,
  - So dynamic cells must be periodically read and rewritten to refresh their state.
- ❑ Static RAMs (SRAMs) are **faster** and **less troublesome**, but require **more area per bit** than their dynamic counterparts (DRAMs).

# Non-Volatile Memory

## ❑ Volatility:

- Some nonvolatile memories are read-only (e.g. mask ROM), but many nonvolatile memories can be written, albeit more slowly than their volatile memories.

## ❑ Types of non-volatile memories:

1. **Mask ROM**: the contents of a mask ROM are **hardwired** during fabrication and cannot be changed.
2. **Programmable ROM (PROM)** is **programmed** once after fabrication by blowing on-chip fuses with a special high programming voltage.
3. **Erasable programmable ROM (EPROM)** is programmed by storing charge on a floating gate.
  - It can be erased by exposure to ultraviolet (UV) light for several minutes to knock the charge off the gate. Then the EPROM can be reprogrammed.
4. **Electrically erasable programmable ROMs (EEPROMs)** are erased in microseconds with on-chip circuitry.
5. **Flash** memories are a variant of EEPROM that erases entire blocks rather than individual bits.
  - Sharing the erase circuitry across larger blocks reduces the area per bit.
  - Because of their good density and easy in-system reprogrammability, Flash memories have replaced other nonvolatile memories in most modern CMOS systems.


# Memory Array Architecture

- ❑ Memory cells can have one or more ports for access.
- ❑ On a read/write memory, each port can be read-only, write-only, or both.
- ❑ A memory array contains  $2^n$  words of  $2^m$  bits each.
  - Total number of bits =  $2^n \times 2^m$  bits
- ❑ memory array containing 16 4-bit words ( $n = 4$ ,  $m = 2$ ).
  - Total number of bits = 64 bits



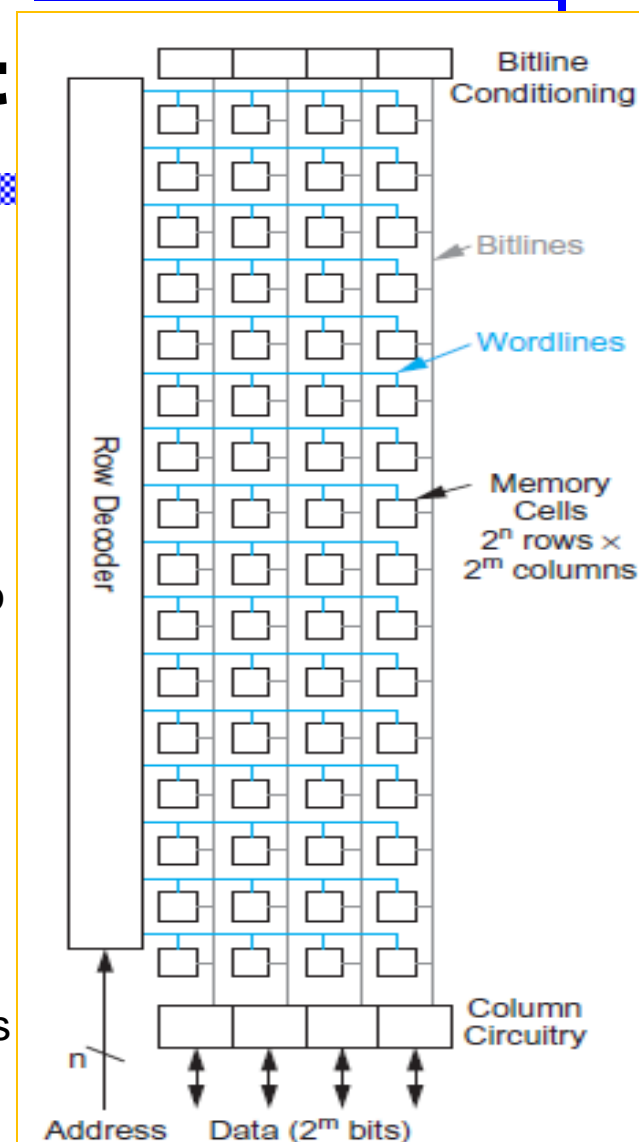
# Memory Array : One row per word and One column per bit

- ❑ The simplest design with one row per word and one column per bit.
- ❑ The **row decoder** uses the address to activate one of the rows by asserting the **wordline**.
- ❑ During a read operation, the cells on this wordline drive the **bitlines**.
- ❑ The **column** circuitry may contain amplifiers or buffers to sense the data.
- ❑ A typical memory array may have thousands or millions of words of only 8–64 bits each, which would lead to a tall, skinny layout that is hard to fit in the chip floorplan and slow because of the long vertical wires.
- ❑ Therefore, the array is often folded into fewer rows of more columns. After folding, each row of the memory contains  $2^k$  words, so the array is physically organized as  $2^{n-k}$  rows of  $2^{m+k}$  columns or bits.


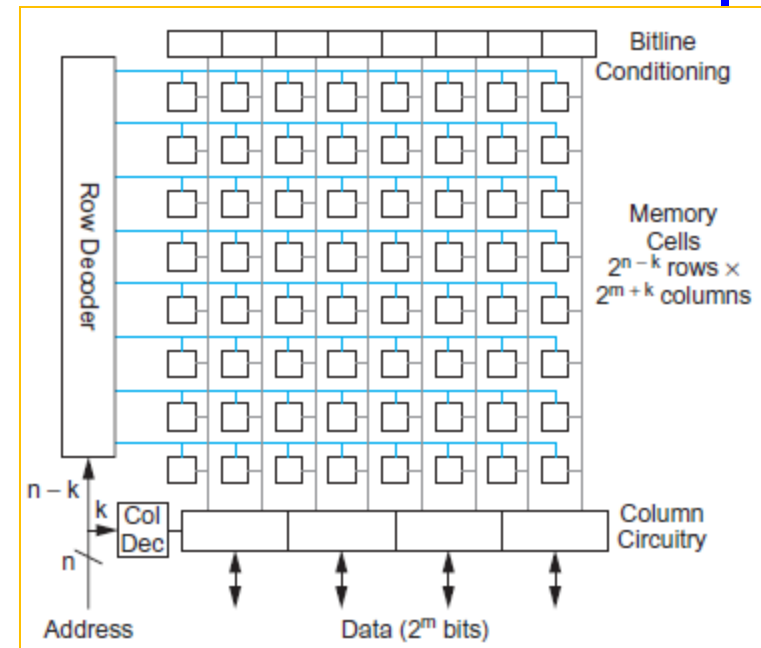
# Memory Array : Two-way Fold

- ❑ The array is physically organized as  $2^{n-k}$  rows of  $2^{m+k}$  columns or bits.
- ❑ The Figure shows a two-way fold ( $k = 1$ ) with eight rows and eight columns.
- ❑ The column decoder controls a multiplexer in the column circuitry to select  $2^m$  bits from the row as the data to access.
- ❑ Larger memories are generally built from multiple smaller sub-arrays so that the wordlines and bitlines remain reasonably short, fast, and low in power dissipation.




**16 4-bit words:**  
**( $n = 4$ ,  $m = 2$ ,  $k=1$ )**

# 12.2 SRAM

- ❑ Static RAMs use a memory cell with internal feedback that retains its value as long as power is applied. It has the following attractive properties:
  - Denser than flip-flops
  - Compatible with standard CMOS processes
  - Faster than DRAM
  - Easier to use than DRAM
- ❑ SRAMs are widely used in: caches, register files, tables and buffers.

 
# SRAM Cell: 12T SRAM Cell

- ❑ Basic building block: SRAM Cell
  - **Holds** one bit of information, like a latch
  - Must be **read and written**
- ❑ 12-transistor (12T) SRAM cell
  - Use a simple latch connected to bitline
  - Large area, so it is not used.
- ❑ Cell size accounts for most of array size
  - Reduce cell size at expense of complexity
  - The small cell size also offers shorter wires and hence lower dynamic power consumption.



 
# SRAM Cell: 6T SRAM Cell

- ❑ 6T SRAM Cell
  - Used in most commercial chips
  - Data stored in cross-coupled inverters
- ❑ Read:
  - Precharge bit, bit\_b
  - Raise wordline
- ❑ Write:
  - Drive data onto bit, bit\_b
  - Raise wordline
- ❑ The central challenges in SRAM design are
  - minimizing its size
  - ensuring that the circuitry holding the state is weak enough to be overpowered during a write, yet strong enough not to be disturbed during a read.




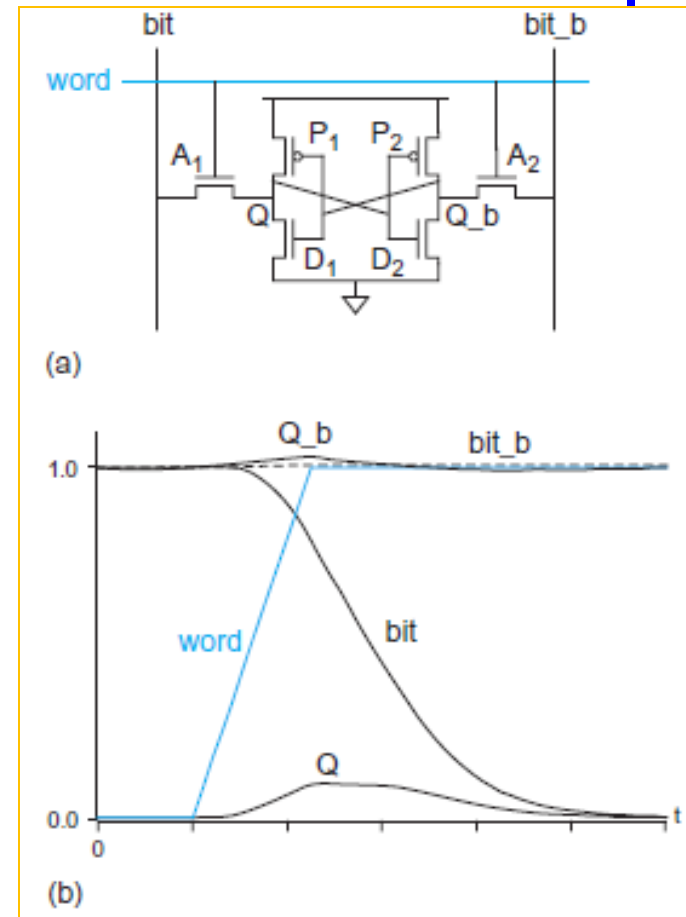
# 12.2.1.1 Read Operation

- ❑ Read operation:
  - Precharge both bitlines high
  - Then turn on wordline
  - One of the two bitlines will be pulled down by the cell
- ❑ Ex:  $Q = 0$ ,  $Q_b = 1$ 
  - bit discharges, bit\_b stays high
  - But Q bumps up slightly
- ❑ *Read stability*
  - P2/D2 must not flip
  - $D1 \gg A1$


 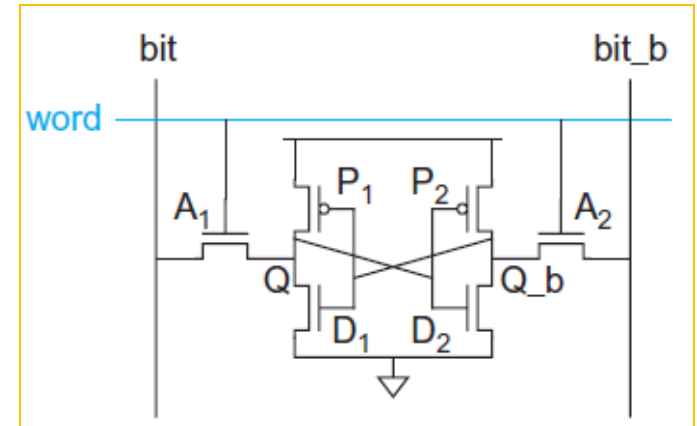
# 12.2.1.2 Write Operation

- ❑ Write operation:
  - Drive one bitline high, the other low
  - Then turn on wordline
  - Bitlines overpower cell with new value
- ❑ Ex:  $Q = 0$ ,  $Q_b = 1$ ,  $\text{bit} = 1$ ,  $\text{bit}_b = 0$ 
  - Force  $Q_b$  low, then  $Q$  rises high
- ❑ *Writability*
  - Must overpower feedback inverter
  - $A_2 \gg P_2$




# 12.2.1.3 Cell Stability

## ❑ Read stability:

- The nMOS pulldown transistor in the cross-coupled inverters must be strongest.
 
## ❑ Writability:



- the access transistors are of intermediate strength, and the pMOS pullup transistors must be weak.




  
# Static Noise Margin

- ❑ The *static noise margin (SNM)* measures how much noise can be applied to the inputs of the two cross-coupled inverters before a stable state is lost (during hold or read) or a second stable state is created (during write).
- ❑ The static noise margin can be determined graphically from a butterfly diagram shown in Figure.
- ❑ The butterfly plot shows two stable states (with one output low and the other high) and one metastable state (with  $V_1 = V_2$ ). A positive value of noise shifts curve I left and curve II up. Excessive noise eliminates the stable state of  $V_1 = 0$  and  $V_2 = V_{DD}$ , forcing the cell into the opposite state.
- ❑ **The static noise margin is determined by the length of the side of the largest square that can be inscribed between the curves.**




---


# REST of the SLIDES Are reading material

# SRAM Column Example

Read



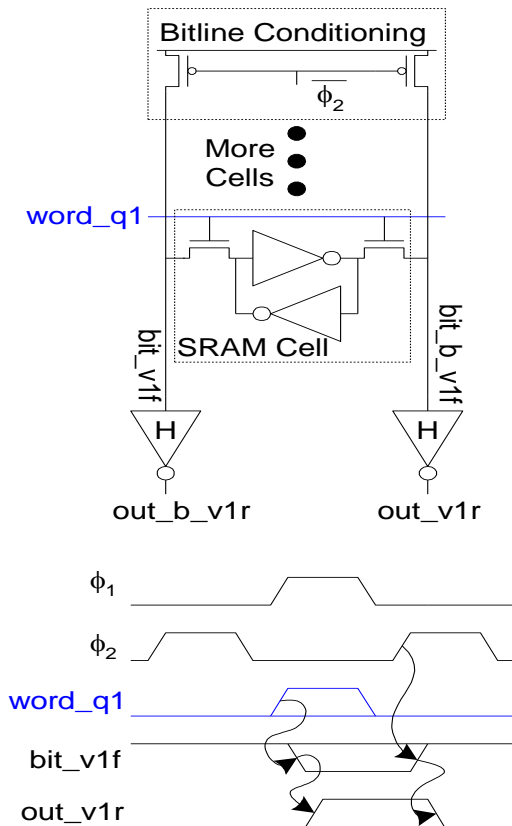


Write

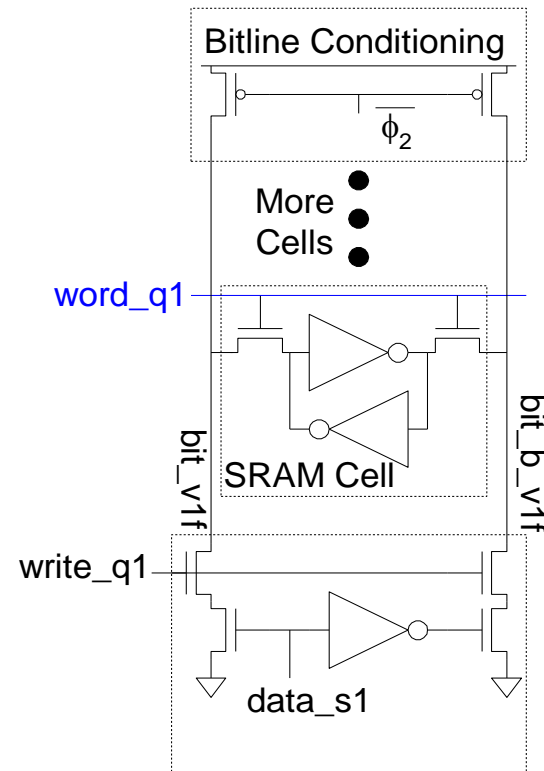

   
# SRAM Layout: Physical Design

- ❑ Cell size is critical (left):  $26 \times 45 \lambda$  (smaller in industry)
- ❑ Tile cells sharing  $V_{DD}$ , GND, bitline contacts (6T:right).



 
# Thin Cell

- ❑ In nanometer CMOS
  - Avoid bends in polysilicon and diffusion
  - Orient all transistors in one direction
- ❑ *Lithographically friendly* or *thin cell* layout fixes this
  - Also reduces length and capacitance of bitlines


 
# Commercial SRAMs


- ❑ Five generations of Intel SRAM cell micrographs.
  - Transition to thin cell at 65 nm
  - Steady scaling of cell area




# Row Circuitry: Decoders

- ❑ Row circuitry consists of decoder & wordline drivers
- ❑  $n:2^n$  decoder consists of  $2^n$   $n$ -input AND gates
  - One needed for each row of memory
  - Build AND from NAND or NOR gates

## Static CMOS


 


## Pseudo-nMOS


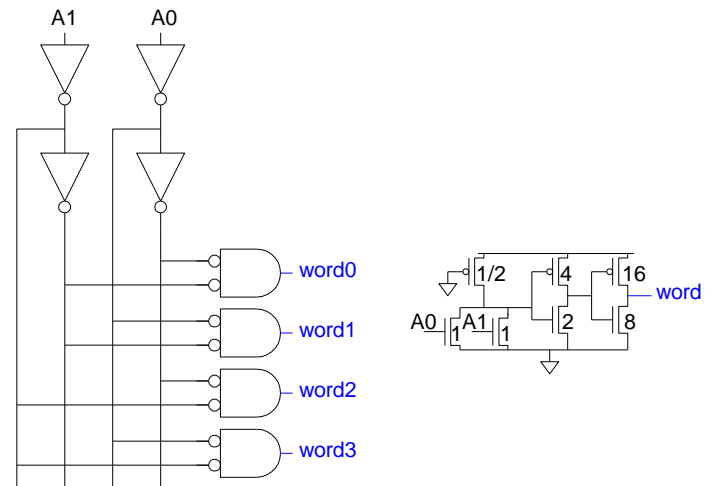


# Row Circuitry: Decoders

## Static CMOS

  

## Pseudo-nMOS

  


- ❑ Wordline must be qualified with clock (shared clock and transistors).



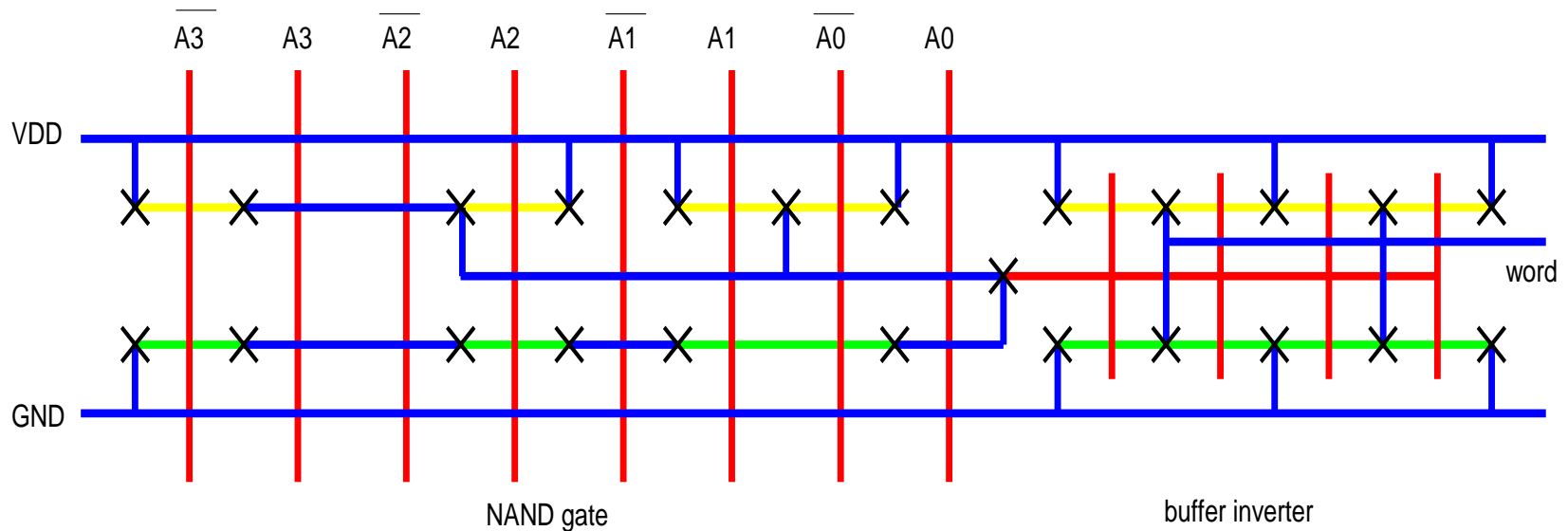
# Decoder Layout

- ❑ Decoders must be pitch-matched to SRAM cell:  
height of decoder gate must match height of the row it drives.
  - Requires very skinny gates



 
# Large Decoders

- ❑ For  $n > 4$ , NAND gates become slow.
  - Break large gates into multiple smaller gates


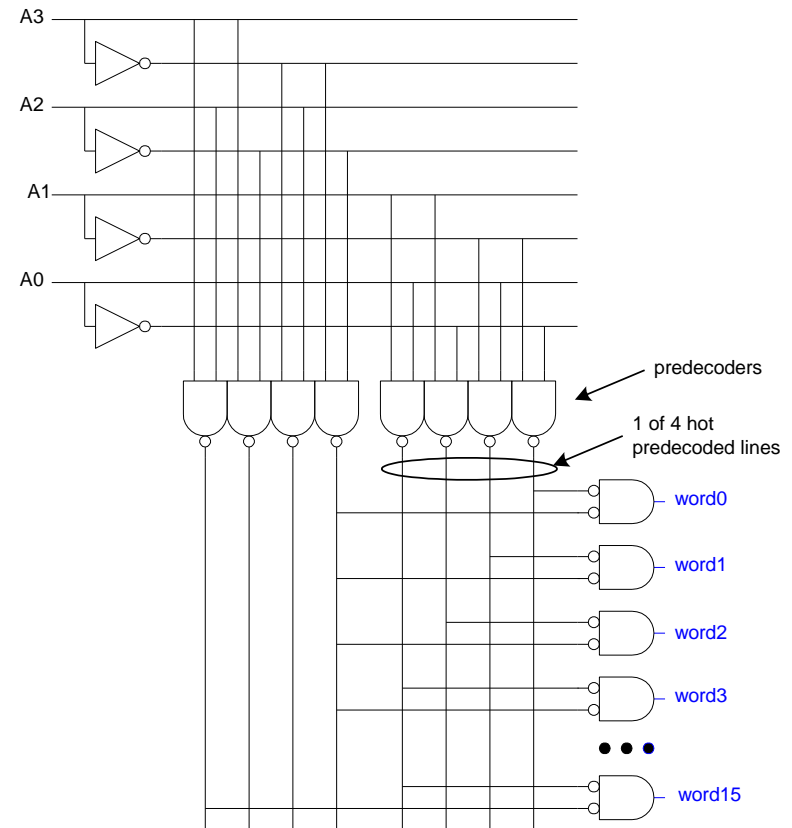
# Predecoding

- ❑ Many of these gates are redundant
  - Factor out common gates into predecoder
  - Saves area
  - Same path effort




# Column Circuitry

---


- ❑ Some circuitry is required for each column
  - Bitline conditioning
  - Write driver
  - Bitline sense amplifiers
  - Column multiplexing
 
# Bitline Conditioning

- ❑ Precharge bitlines high before reads or writes



 - ❑ Equalize bitlines to minimize voltage difference when using sense amplifiers



# Bitline Sense Amplifiers


- ❑ Bitlines is classified: large-signal (single-ended sensing) or small-signal. (differential sensing).
- ❑ Large-signal: bitline swings between  $V_{dd}$  and GND.
- ❑ Small-signal: one of the two bitlines changes by a small amount to save delay and reduce energy consumption.

# Bitline Sense Amplifiers

- ❑ Bitlines have many cells attached
  - Ex: 32-kbit SRAM has 128 rows x 256 cols
  - 128 cells on each bitline
- ❑  $t_{pd} \propto (C/I) \Delta V$ 
  - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
  - Discharged slowly through small transistors (small I)
- ❑ *Sense amplifiers* are triggered on small voltage swing (reduce  $\Delta V$ )
 
# Differential Pair Amp


- ❑ Differential pair requires no clock
- ❑ But always dissipates static power
- ❑ Consumes a significant amount of DC power.





 
# Clocked Sense Amp

- ❑ Clocked sense amp saves power (consumes power only while activated).
- ❑ Requires sense\_clk after enough bitline swing
- ❑ Isolation transistors cut off large bitline capacitance, regenerative feedback to make one output high and the other low.


 
# Twisted Bitlines

- ❑ Sense amplifiers also amplify noise
  - Coupling noise is severe in modern processes
  - Try to couple equally onto bit and bit\_b
  - Done by *twisting* or *transposing* bitlines




# Column Multiplexing

- ❑ Recall that array may be folded for good aspect ratio
- ❑ Ex: 2 kword x 16 folded into 256 rows x 128 columns
  - Must select 16 output bits from the 128 columns
  - Requires 16 8:1 column multiplexers



 
# Tree Decoder Mux

- ❑ Column mux can use pass transistors
  - Use nMOS only, precharge outputs
- ❑ One design is to use k series transistors for  $2^k:1$  mux
  - No external decoder logic needed


 
# Single Pass-Gate Mux

- ❑ Or eliminate series transistors with separate decoder




# Multiple Ports

- ❑ We have considered single-ported SRAM
  - One read or one write on each cycle
- ❑ *Multiported* SRAM are needed for register files
- ❑ Examples:
  - Multicycle MIPS must read two sources or write a result on some cycles
  - Pipelined MIPS must read two sources and write a third result each cycle
  - Superscalar MIPS must read and write many sources and results each cycle
 
# Dual-Ported SRAM

- ❑ Simple dual-ported SRAM
  - Two independent single-ended reads
  - Or one differential write



- ❑ Do two reads and one write by time multiplexing
  - Read during ph1, write during ph2




# Multi-Ported SRAM

- ❑ Adding more access transistors hurts read stability
- ❑ Multiported SRAM isolates reads from state node
- ❑ Differential read ports double the number of read bitlines and transistors.
- ❑ Single-ended bitlines save area
- ❑ Multiple write ports simply attach the ports to the state node.

# Multi-Ported SRAM

- 3 write ports and 4 read ports:

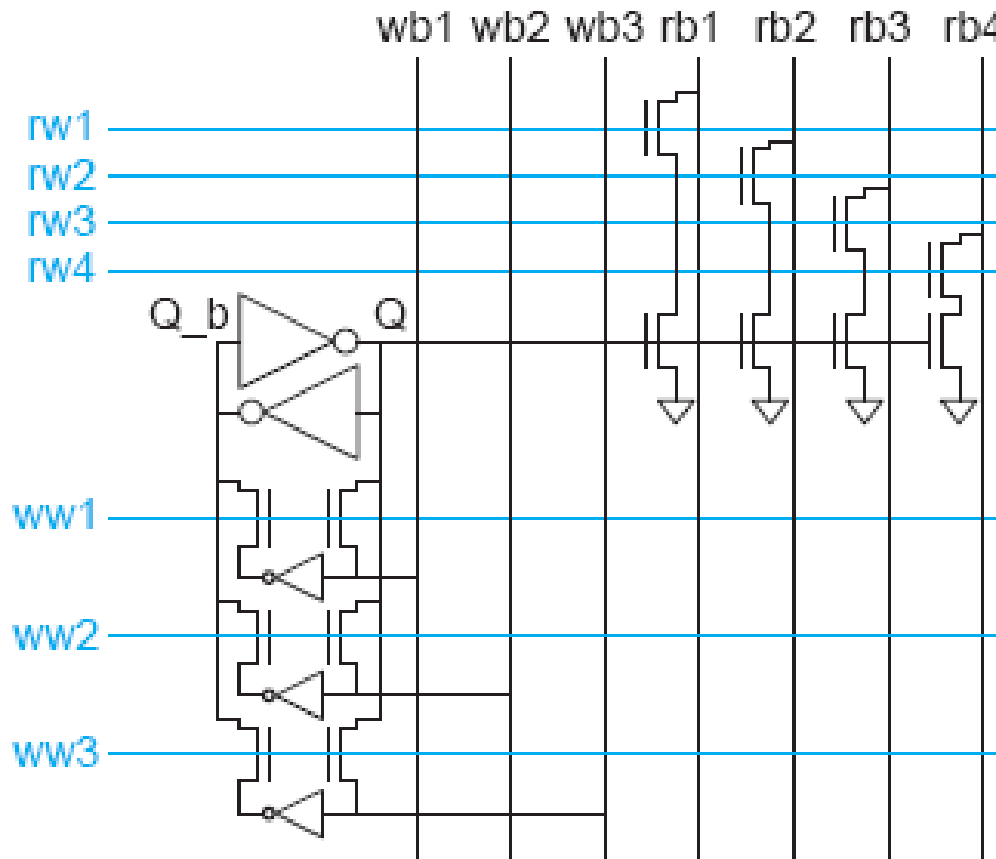

# Large SRAMs

- ❑ Large SRAMs are split into banks or subarrays for speed and reduce power
- ❑ Ex: UltraSparc 512KB cache
  - 4 128 KB subarrays
  - Each have 16 8KB banks
  - 256 rows x 256 cols / bank
  - 60% subarray area efficiency
  - Also space for tags & control

